



# Arithmetic Units

---

KECE207 Digital System Design (Spring 2020)

Prof. Seon Wook Kim  
School of EE, Korea University  
<http://compiler.korea.ac.kr>  
[seon@korea.ac.kr](mailto:seon@korea.ac.kr)

# Contents

---


- **Binary**
  - Adders/Subtractors
  - Multipliers
- **BCD**
  - Adder
- **Floating-point (bfloat16)**
  - Multiplier
  - Adder

# Half Adder (HA)

- Add two 1-bit binary inputs

Inputs		Outputs	
X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Truth Table of Half Adder

 

Logic Diagram of Half Adder


- How about using 2-to-4 decoders & 2-to-1 multiplexers?

# Full Adder (FA)

- Add three 1-bit binary inputs.


Inputs			Outputs	
X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Truth Table of Full Adder

 

$$S = \bar{X}\bar{Y}Z + \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z} + XYZ$$

$$= X \oplus Y \oplus Z$$

 

$$C = XY + XZ + YZ$$


$$= XY + Z(X\bar{Y} + \bar{X}Y)$$

$$= XY + Z(X \oplus Y)$$

Maps for Full Adder

- $X = A_i$ ,  $Y = B_i$ ,  $Z = C_i$ ,  $C = C_{i+1}$ ,  $S = S_i$


# 4-bit Binary Ripple Carry Adder (RCA)

 

- **Critical path?**
  - 4 FA delays
- **How about longer bit adders? Like 32-bit?**

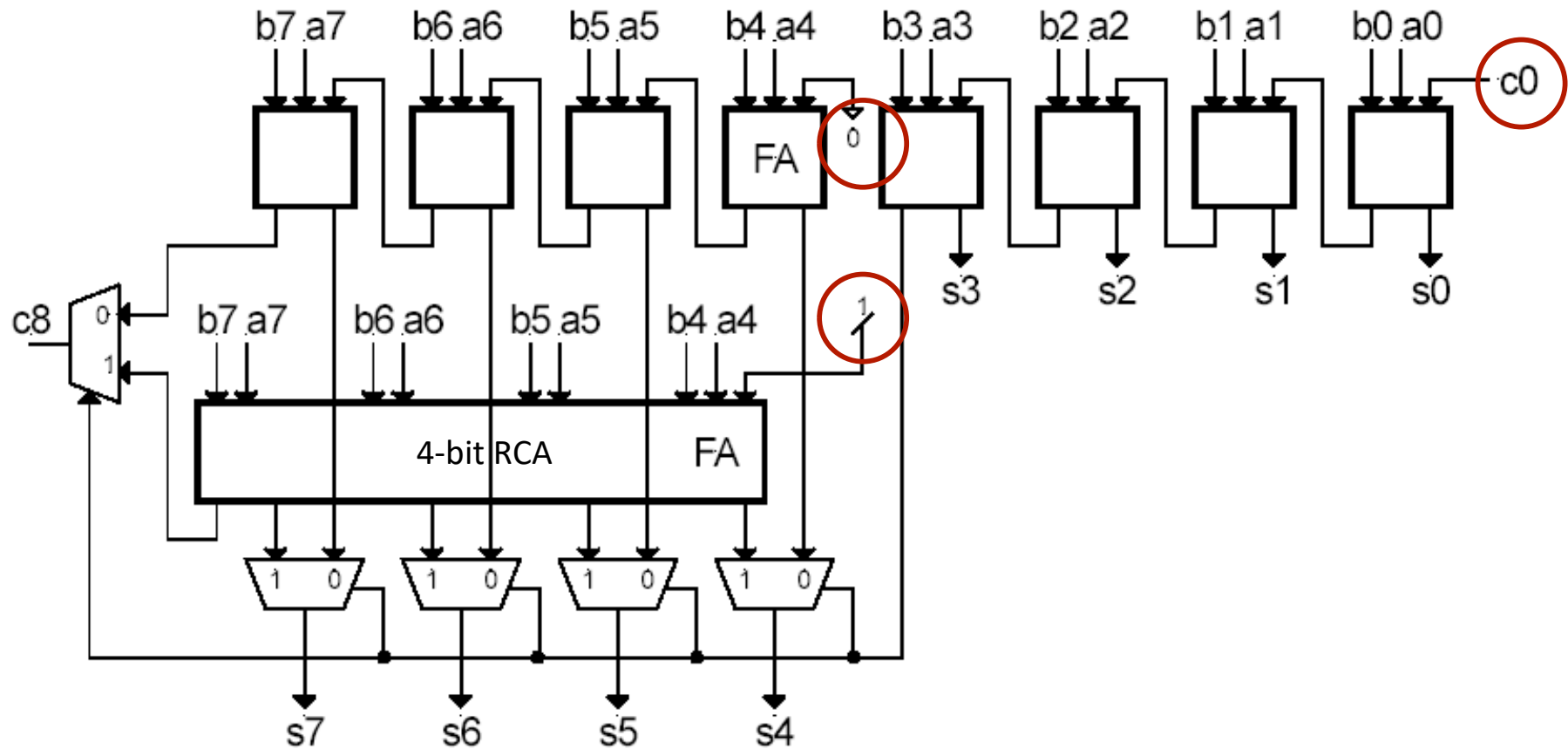
# Carry Select Adder (CSA)

- **Delay** =  $\text{Delay}_{\text{ripple\_carry}(8\text{bit})}/2 + \text{Delay}_{\text{MUX}}$
- **Cost** =  $1.5 * \text{Cost}_{\text{ripple\_carry}(4\text{bit})} + \text{Cost}_{\text{MUX}}$


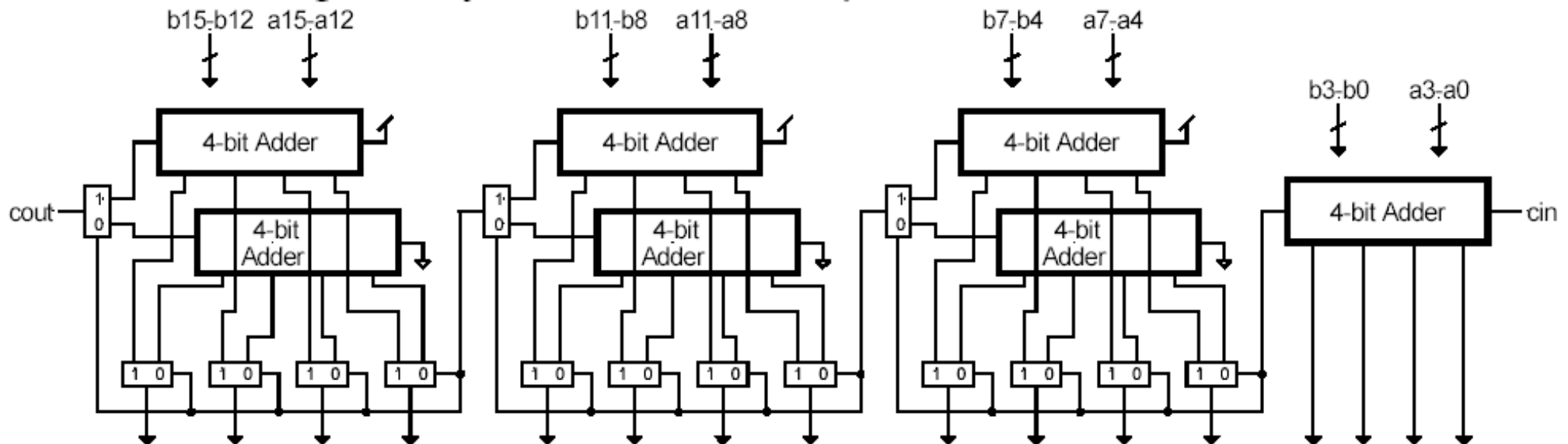
# Extending CSA to multiple blocks

- N-bit CSA:  $\text{Sqrt}(N)$  stages of  $\text{sqrt}(N)$  bits




- What is the optimal # of blocks and # of bits/block?
  - If # blocks are too large, the delay is dominated by total MUX delay.
  - If # blocks are too small, the delay is dominated by adder delay.
 
# Carry Lookahead Adder (CLA)

- **PFA (Partial Full Adder)**

- Extract carry propagation path from FA's.
- Input:  $A_i$ ,  $B_i$ ,  $C_i$
- Output:  $P_i$ ,  $G_i$ ,  $S_i$



- **Propagate function:  $P_i = A_i \oplus B_i$**

- $P_i = 1$ : an incoming carry is propagated through the bit position from  $C_i$  to  $C_{i+1}$ .
- $P_i = 0$ : carry propagation through the bit position is blocked.

- **Generate function:  $G_i = A_i B_i$**

- $G_i = 1$ : the carry output from the position is 1, regardless of the value of  $P_i$ , so carry has been generated in the position.
- $G_i = 0$ :  $C_{i+1} = 0$  if the carry propagated through the position from  $C_i$  is also 0.




# CLA Boolean Expression


---

- $C_1 = A_0B_0 + C_0(A_0 \oplus B_0) = G_0 + C_0P_0$
- $C_2 = A_1B_1 + C_1(A_1 \oplus B_1) = G_1 + C_1P_1$   
 $= G_1 + (G_0 + C_0P_0) P_1$   
 $= G_1 + P_1 G_0 + P_1P_0C_0$
- .....
- $C_n = G_{n-1} + P_{n-1} G_{n-2} + P_{n-1} P_{n-2} G_{n-3} + \dots + P_{n-1} P_{n-2} \dots P_1 G_0 + P_{n-1} P_{n-2} \dots P_1 P_0 C_0$


# 4-bit Adder with Carry Lookahead

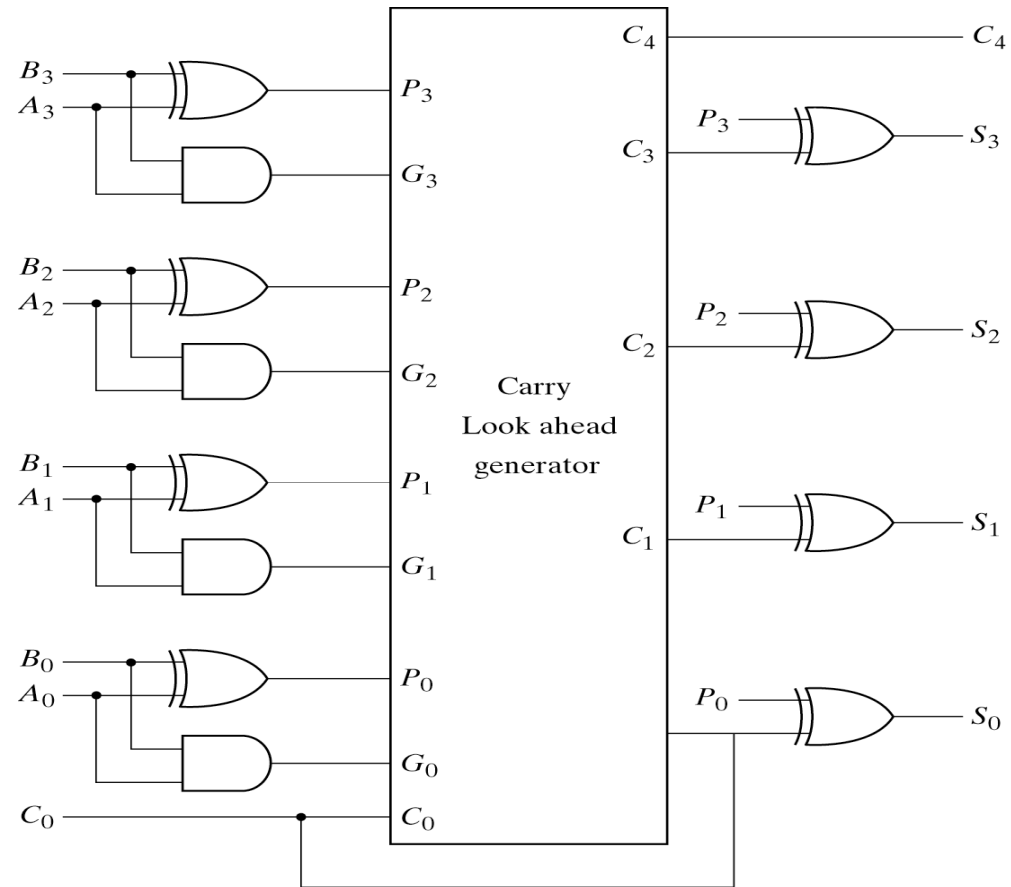

# CLA Generator

 


Ripple.  
Slow but Simple

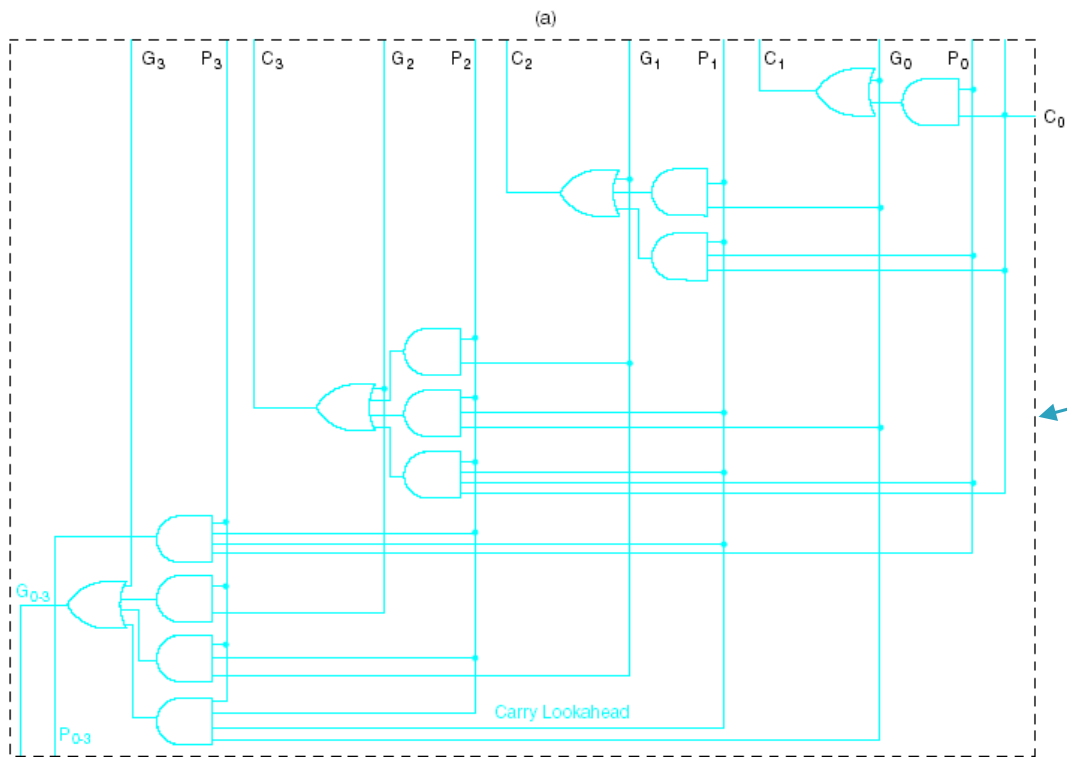

Fast, but Complex

Development of a Carry Lookahead Adder


# 4-bit Binary Adder & Subtractor

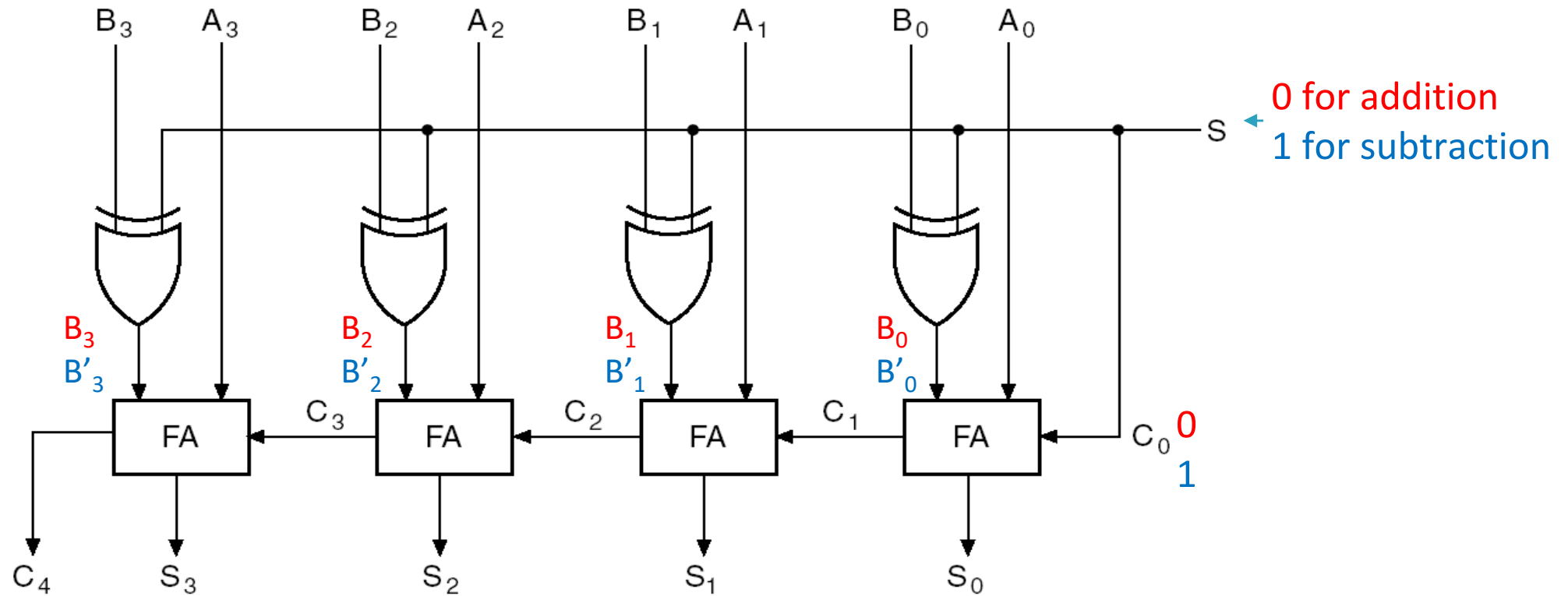

$$\begin{aligned}
 \bullet \quad A_3A_2A_1A_0 - (B_3B_2B_1B_0) &= A_3A_2A_1A_0 + (-B_3B_2B_1B_0) \\
 &= A_3A_2A_1A_0 + (B'_3B'_2B'_1B'_0 + 1)
 \end{aligned}$$

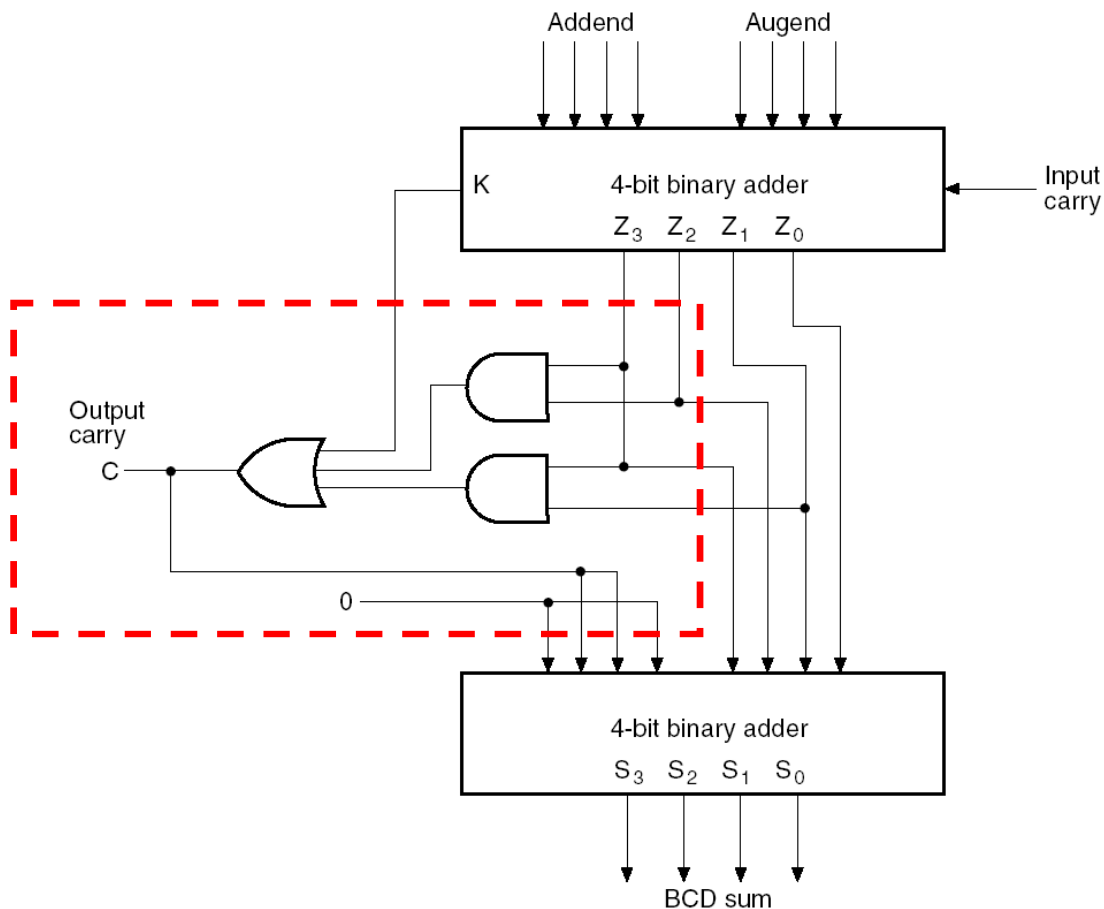
# Decimal Adder (BCD Adder)

- Binary numbers 1010 ~ 1111 need to be corrected
- 1010, 1011, 1100, 1101, 1110, 1111
- If  $C = K + Z_1Z_3 + Z_2Z_3$ , add 0110 to the binary sum




# 2-bit x 2-bit Unsigned Binary Multiplier

		$B_1$	$B_0$
	$A_1$	$A_0$	
	$A_0B_1$	$A_0B_0$	
$A_1B_1$	$A_1B_0$		
$C_3$	$C_2$	$C_1$	$C_0$

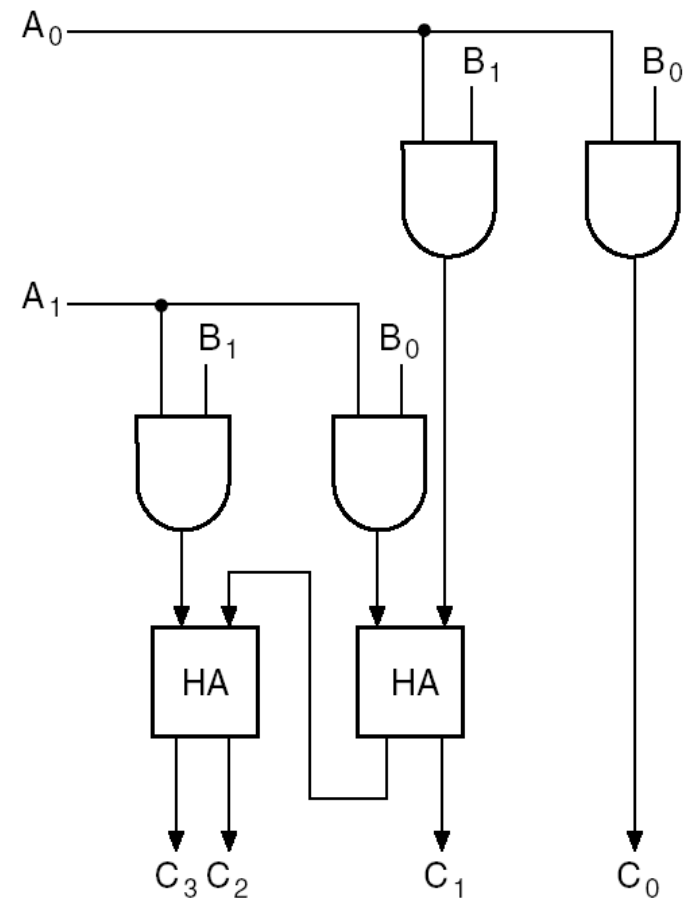
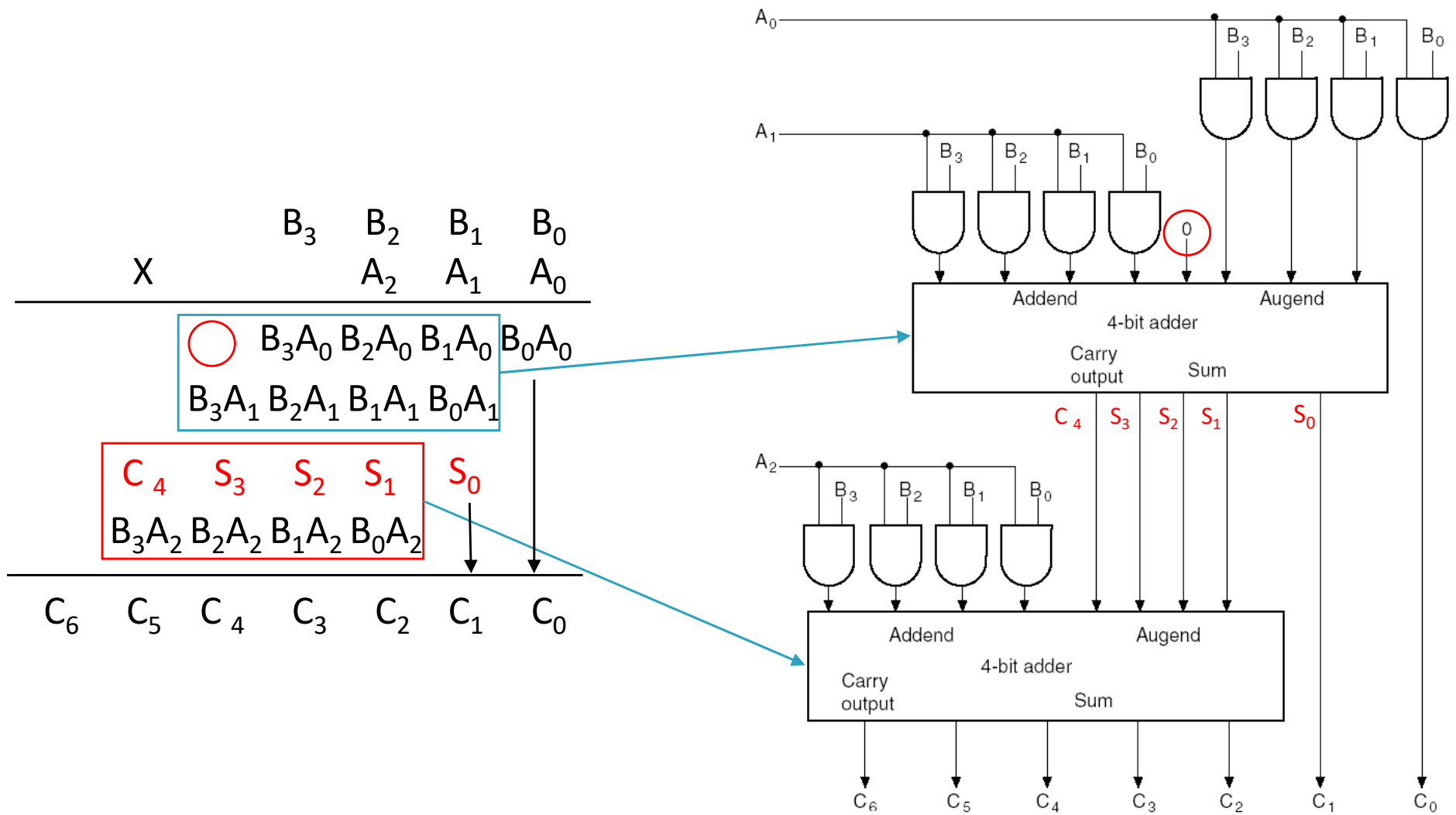
# 4-bit x 3-bit Unsigned Binary Multiplier




A 4-Bit by 3-Bit Binary Multiplier
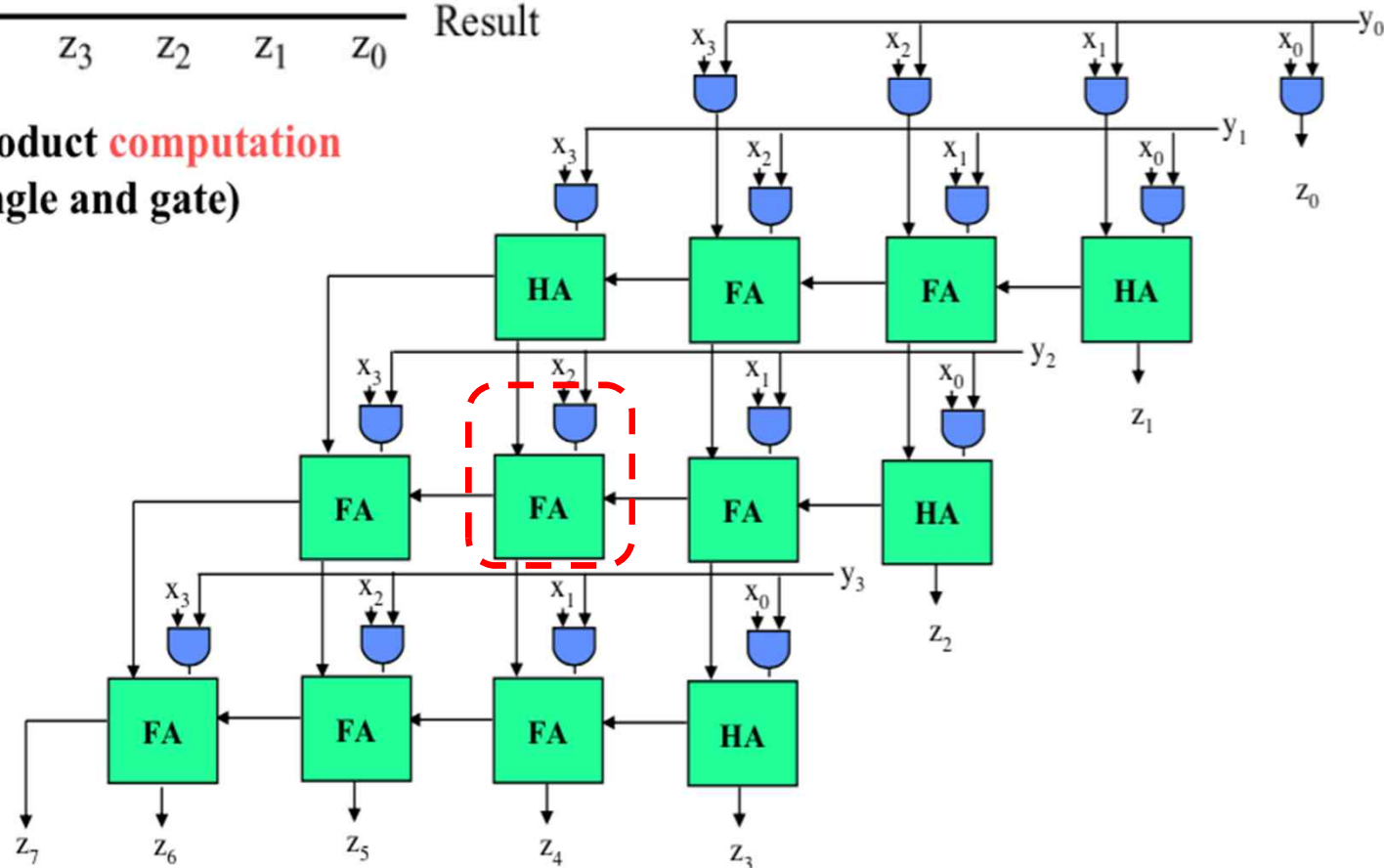
# 4-bit x 4-bit Unsigned Array Multiplier

$$\begin{array}{r}
 \begin{array}{cccc}
 & x_3 & x_2 & x_1 & x_0 & \text{Multiplicand} \\
 \times & y_3 & y_2 & y_1 & y_0 & \text{Multiplier} \\
 \hline
 & x_3y_0 & x_2y_0 & x_1y_0 & x_0y_0 & \\
 x_3y_1 & x_2y_1 & x_1y_1 & x_0y_1 & & \text{Partial Product} \\
 x_3y_2 & x_2y_2 & x_1y_2 & x_0y_2 & & \\
 + \ x_3y_3 & x_2y_3 & x_1y_3 & x_0y_3 & & \\
 \hline
 z_7 & z_6 & z_5 & z_4 & z_3 & z_2 & z_1 & z_0 & \text{Result}
 \end{array}
 \end{array}$$

➤ Partial product **computation** is simple (single and gate)



Spring 2006, MIT Courseware



# Signed Binary Multiplier

- Two steps
  - ① **Sign extend** both integers to twice as many bits.
  - ② Then take the correct number of result bits from the least significant portion of the result.
- 4-bit examples**

$$-1 \times -7 = 7$$

$$\begin{array}{r} \phantom{1111} 1111 \\ \times \phantom{1111} 1001 \\ \hline 11111111 \\ 00000000 \\ 00000000 \\ 11111111 \\ 11111111 \\ 11111111 \\ 11111111 \\ 11111111 \\ \hline 1 \dots 00000000111 \end{array}$$

$$3 \times -5 = -15$$

$$\begin{array}{r} \phantom{0000} 0011 \\ \times \phantom{0000} 1011 \\ \hline 00000011 \\ 00000011 \\ 00000000 \\ 00000011 \\ 00000011 \\ 00000011 \\ 00000011 \\ 00000011 \\ \hline 1011110001 \end{array}$$


# Signed Binary Multiplier (why?)

- $(-3) \times (-2)$ : Ignore the overflow & Expand the dimension!

$$\begin{array}{r} 111\ 101 \\ \times 111\ 110 \\ \hline 000\ 000 \\ 1111\ 01 \\ 11110\ 1 \\ 111101 \\ \dots \\ \hline \dots\ 000\ 110 \end{array}$$
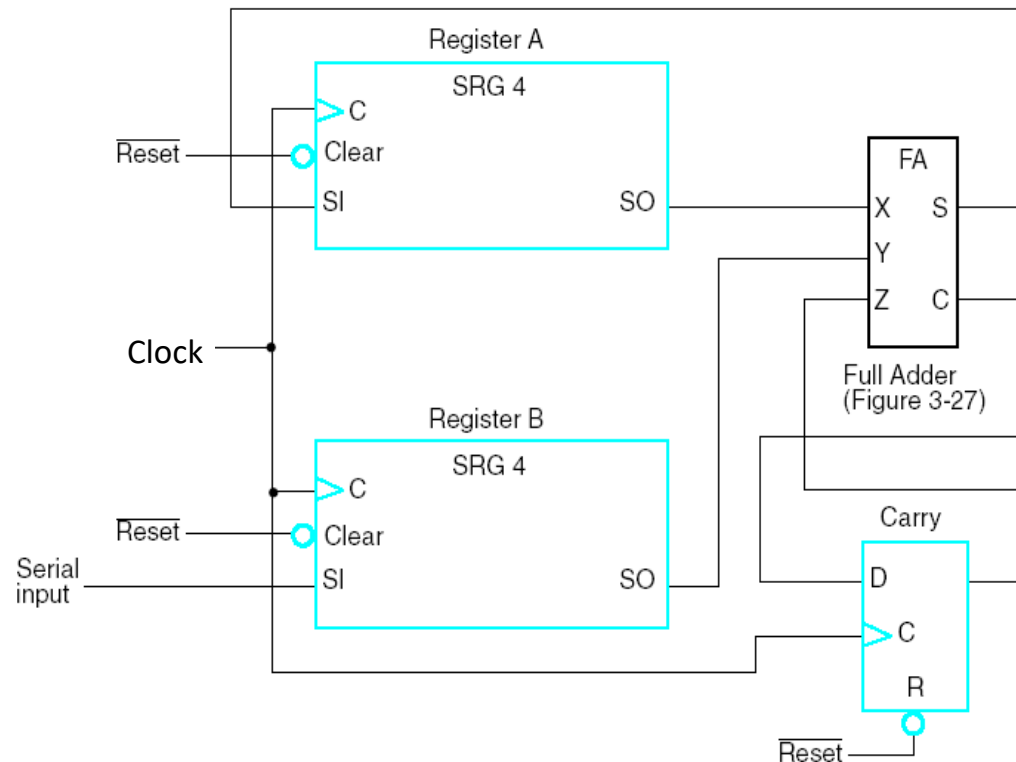
# Bit Serial Adder: A+B


- A, B are held in shift registers.
- Initially, Carry FF is set to 0.
- Shift A and B right once per clock cycle.
- Take n clock cycles.



# Bit Serial Adder (Another Approach)

State Table for Serial Addder

Present State	Inputs		Next State	Output	Flip-Flop Inputs	
					$J_Q$	$K_Q$
$Q$	$x$	$y$	$Q$	$S$		
0	0	0	0	0	0	X
0	0	1	0	1	0	X
0	1	0	0	1	0	X
0	1	1	1	0	1	X
1	0	0	0	1	X	1
1	0	1	1	0	X	0
1	1	0	1	0	X	0
1	1	1	1	1	X	0

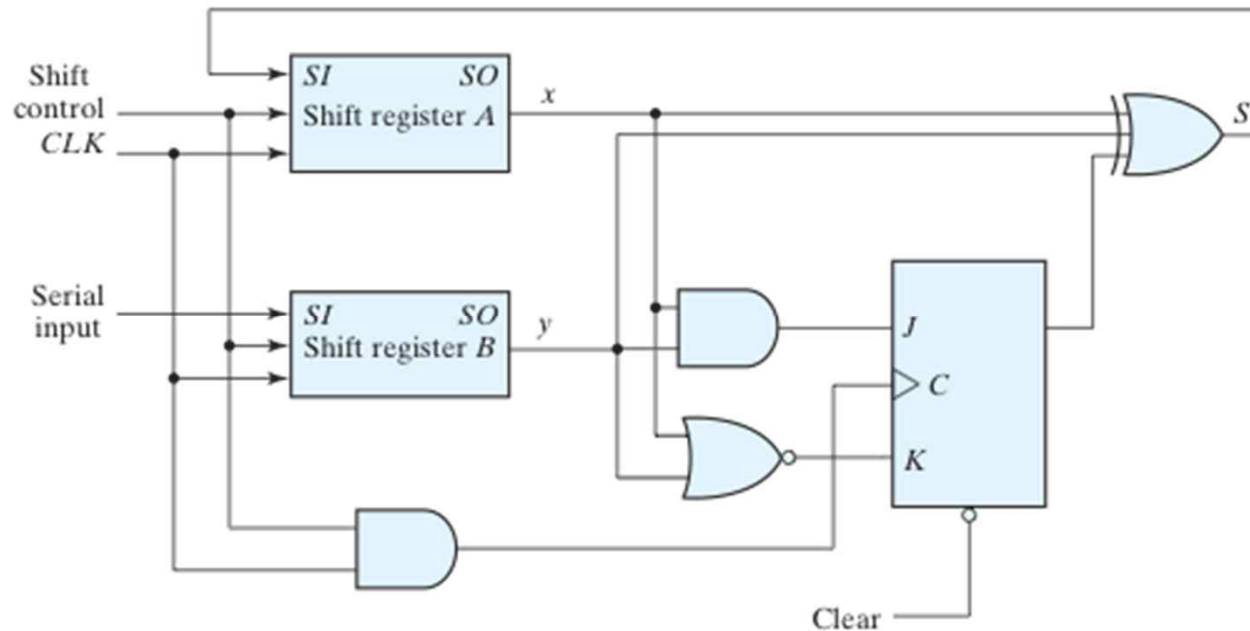


# Shift-and-Add Multiplier

## • Algorithm

- ① Step 1:  $A \leftarrow 0$ ,  $B \leftarrow \text{multiplicand}$ ,  $Q \leftarrow \text{multiplier}$
- ② Step 2: If  $Q_0 == 1$  then add  $B$  to  $A$
- ③ Step 3: Shift  $A|Q$  right once.
- ④ Step 4: Repeat Steps 2 and 3  $n-1$  times.
- ⑤ Step 5:  $A|Q$  has product.


	B				Q				Initial Values	
	1 1 0 1				1 0 1 1					
C	A									
0	0 0 0 0				1 0 1 1					
0	1	1	0	1	1	0	1	1	Add Shift	First Cycle
0	0	1	1	0	1	1	0	1		
1	0	0	1	1	1	1	0	1	Add Shift	Second Cycle
0	1	0	0	1	1	1	1	0		
0	1	0	0	1	1	1	1	0	No Add	Third Cycle
0	0	1	0	0	1	1	1	1	Shift	
1	0	0	0	1	1	1	1	1	Add Shift	Fourth Cycle
0	1	0	0	0	1	1	1	1		
Final Product										

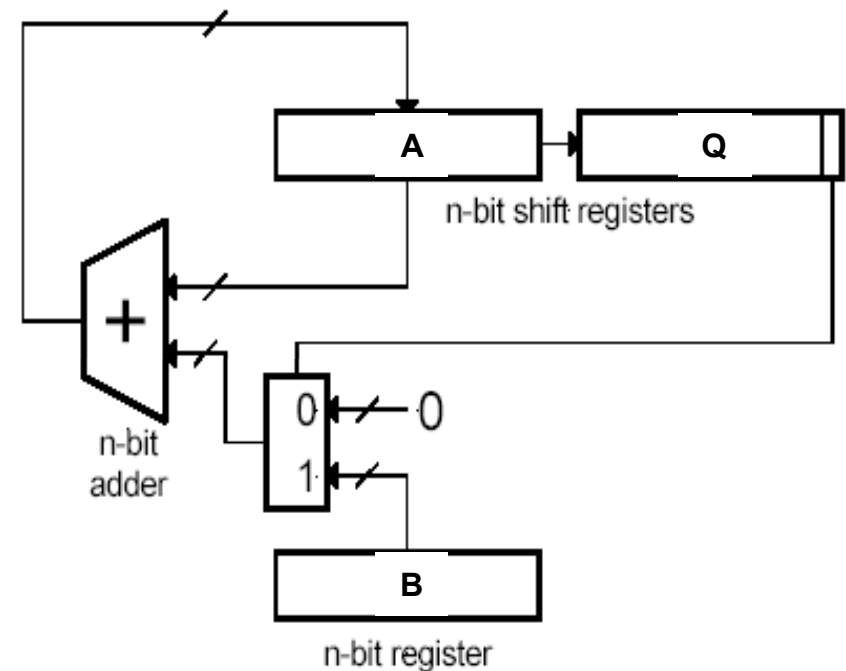

# Floating-Point (bfloat16)

In 1938, Konrad Zuse of Berlin completed the Z1, the first binary, programmable mechanical computer; it uses a 24-bit binary floating-point number representation with a 7-bit signed exponent, a 17-bit significand (including one implicit bit), and a sign bit.

## • fp32 ↔ bfloat16

 


## • Bfloat16

- $E_{\min} = 01_H - 7F_H = -126$
- $E_{\max} = FE_H - 7F_H = 127$
- Exponent bias =  $7F_H = 127$

## Examples:

- ①  $0\ 01111111\ 00000000 = 1$
- ②  $1\ 10000000\ 00000000 = -2$

Exponent	Significand zero	Significand non-zero	Equation
00 <sub>H</sub>	zero, -0	subnormal numbers	$(-1)^{\text{signbit}} \times 2^{-126} \times 0.\text{significandbits}$
01 <sub>H</sub> , ..., FE <sub>H</sub>	normalized value		$(-1)^{\text{signbit}} \times 2^{\text{exponentbits}-127} \times 1.\text{significandbits}$
FF <sub>H</sub>	±infinity	NaN (quiet, signaling)	

 

- **Positive and negative infinity**

- +inf = 0 11111111 00000000
- -inf = 1 11111111 00000000

- **Not a Number (NaN)** where at least one of *k*, *l*, *m*, *n*, *o*, *p*, or *q* is 1.

- +NaN = 0 11111111 klmnopq
- -NaN = 1 11111111 klmnopq

- **Zeros**

- +0 = 0 00000000 00000000
- -0 = 1 00000000 00000000

- **Positive**

- Max = 0 11111110 11111111 =  $(2^8-1) \times 2^{-7} \times 2^{127} = 3.38953139 \times 10^{38}$
- Min = 0 00000001 00000000 =  $2^{-126} = 1.175494351 \times 10^{-38}$

Exponent	Significand zero	Significand non-zero	Equation
00 <sub>H</sub>	zero, -0	subnormal numbers	$(-1)^{\text{signbit}} \times 2^{-126} \times 0.\text{significandbits}$
01 <sub>H</sub> , ..., FE <sub>H</sub>	normalized value		$(-1)^{\text{signbit}} \times 2^{\text{exponentbits}-127} \times 1.\text{significandbits}$
FF <sub>H</sub>	±infinity	NaN (quiet, signaling)	

# Multiplication: Algorithm

---

- $X = (-1)^{S_x} M_x * 2^{E_x}$ ,  $Y = (-1)^{S_y} M_y * 2^{E_y}$
- $X * Y = ((-1)^{S_x} * (-1)^{S_y}) * (M_x * M_y) * 2^{E_x+E_y}$

- **Steps**

- ① Check Zeros

- If one or both operands is equal to zero, return the result as zero.

- ② Compute the sign of the result,  $S_x \square S_y$

- ③ Multiply mantissa,  $M_x * M_y$

- ④ Add exponents:  $E_x + E_y - 127$

- ⑤ Normalize the result

- Left shift the result mantissa & decrease the result exponent (e.g., 0.001xx...)
    - Right shift the result mantissa & increase the result exponent (e.g., 10.1xx...)

- ⑥ Check result

- If larger/smaller than maximum exponent allowed return exponent overflow/underflow



# Multiplication: Example

- **Suppose**

- $X = 0\ 01111111\ 00000000 = 1$

- $Y = 1\ 10000000\ 00000000 = -2$

- **Steps**

- ① N/A

- ②  $S_x \square S_y = 1$

- ③  $M_x = 1.0000000$ ,  $M_y = 1.0000000$ . Don't forget the hidden bit.

- $M_x * M_y = 1.000000000000000$

- ④  $E_x = 01111111$ ,  $E_y = 10000000$ :  $E_x + E_y - 127 = 10000000$

- ⑤ Normalize the result

- N/A

- ⑥ N/A

- **Result:  $1\ 10000000\ 00000000 = -2$**

# Addition and Subtraction: Algorithm

---

- ① **Compare the exponent of the two numbers & shift the smaller number to the right until its exponent matches the larger exponent.**
- ② **Add the mantissas**
- ③ **Normalize the result**
  - Left shift the result mantissa & decrease the result exponent (e.g., 0.001xx...)
  - Right shift the result mantissa & increase the result exponent (e.g., 10.1xx...)
- ④ **Check result**
  - If larger/smaller than maximum exponent allowed return exponent overflow/underflow
- ⑤ **If the mantissa is zero, then set the exponent to zero**

# Addition: Example

---

- **Suppose**

- $X = 0\ 01111111\ 0100000 = 1.25$

- $Y = 0\ 01111101\ 0000000 = 0.25$

- **Steps**

- ① Set  $Y = 0\ 01111111\ 0100000$

- ②  $1.0100000 + 0.0100000 = 1.1000000$

- ③ N/A

- ④ N/A

- ⑤ N/A

- **Result:  $0\ 01111111\ 1000000 = 1.5$**

- More? Divisor.....